

A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a blue gradient background, resembling a circuit board or a tree structure.

# DIGITAL DESIGN

LAB9 SYNCHRONOUS SEQUENTIAL CIRCUIT-LATCH-FLIPFLOP

WANGW6@SUSTECH.EDU.CN


# LAB9

- Synchronous sequential circuit
  - Latch
  - Flip Flops (key point of lab9)
- Verilog
  - `always@(posedge clk)` , `always@(negedge clk)` vs `always@*`
  - blocking assignment vs non-blocking assignment
- Practice

# RECALL: 4-2 PRIORITY-EN-CODER

```
//4-2 priority-encoder
module pri_encoder(
input I0, I1, I2, I3,
output reg [1:0] Y
);
    always @* begin
        case ( {I3, I2, I1, I0} )
            4'bxxx0: Y=2'b00;
            4'bxxx1: Y=2'b01;
            4'bx011: Y=2'b10;
            4'b0111: Y=2'b11;
        endcase
    end
endmodule
```

通配性

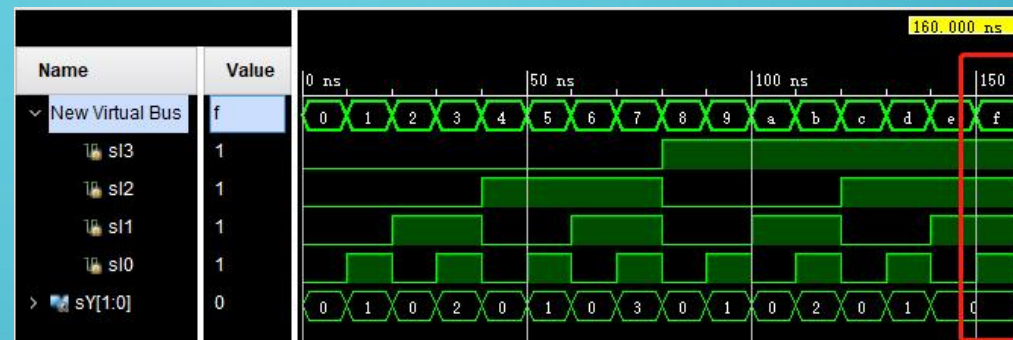


If there is no 'default' branch and the branch(e.g. 4'b1111 in this demo) is not list in the branches of the 'case', the circuit state will remain unchanged, and then a **latch** will be generated to save the state.

# LATCH

- The schematic on the right hand is the schematic of the synthesized design generated by vivado.
- LDCE**: transparent Data **Latch** with Asynchronous Clear and Gate Enable


组合逻辑如果不在设计代码把所有场景罗列出来 否则会自动添加一些时序电路

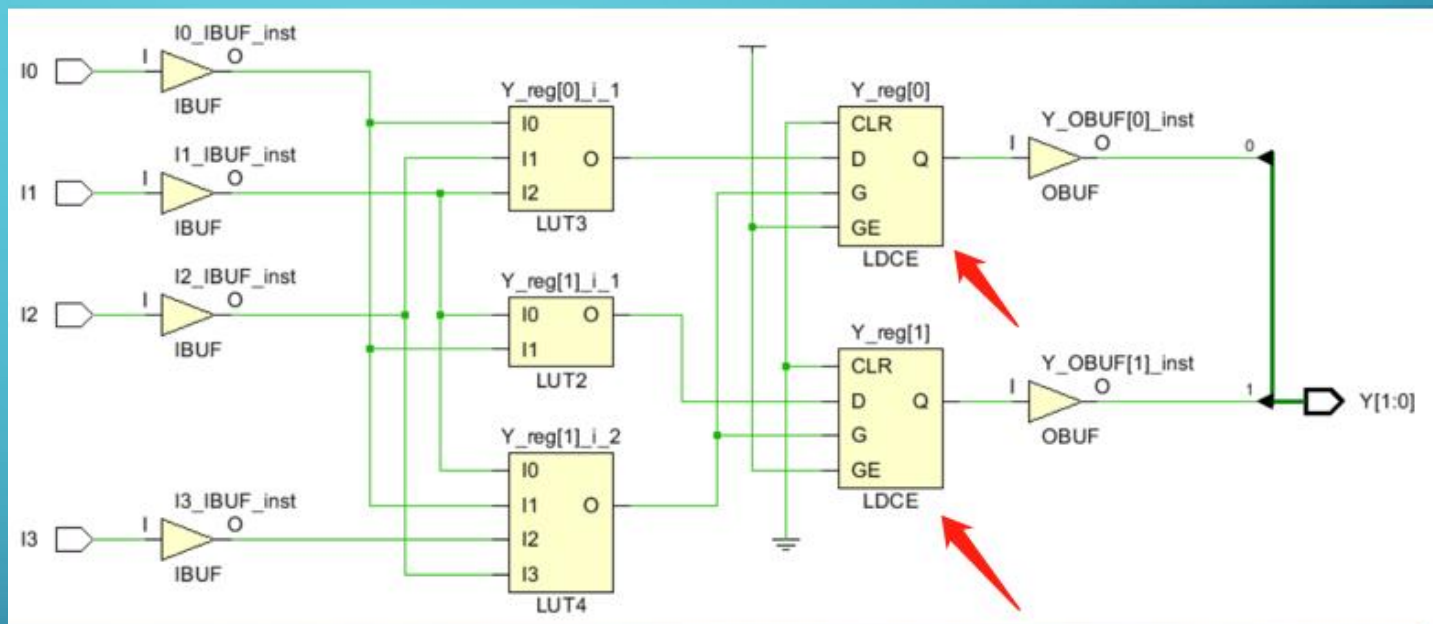

For more information on LDCE, please refer to *Xilinx 7 Series FPGA Libraries Guide for Schematic Design*
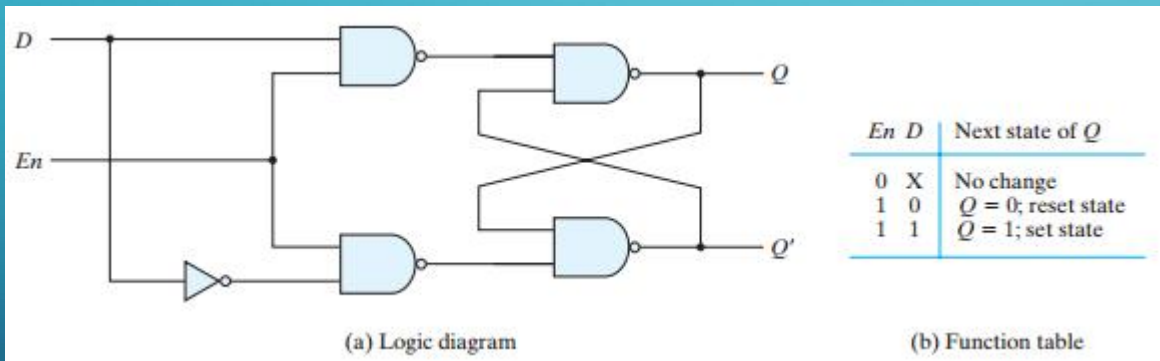
# D LATCH

- Latch: the simplest binary memory elements, static device composed of gates. When the input changes, the output changes immediately.




```
module D_Latch(  
    input En, D,  
    output reg Q,  
    output wire nQ  
);  
    assign nQ = ~Q;  
    always @*  
        if(En)  
            Q = D;  
        else  
            Q = Q;  
endmodule
```




# D LATCH

- Schematic of RTL analysis:

| En | D | Next state of $Q$     |
|----|---|-----------------------|
| 0  | X | No change             |
| 1  | 0 | $Q = 0$ ; reset state |
| 1  | 1 | $Q = 1$ ; set state   |

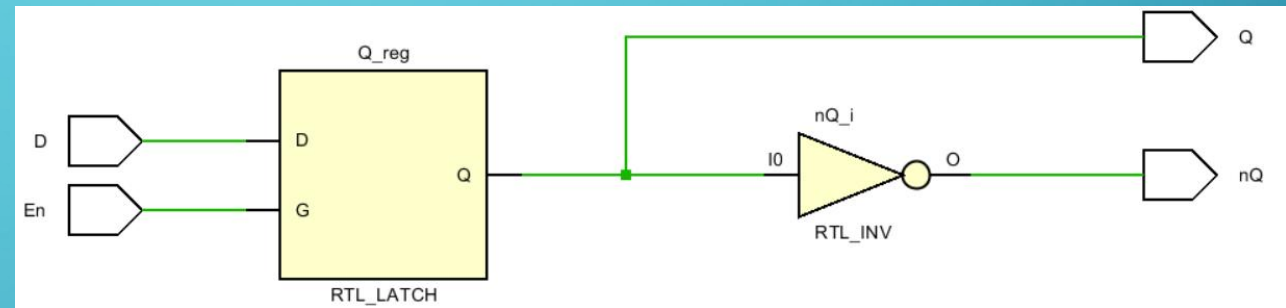

- Simulation result of D Latch

 

# FLIP FLOP ( DESIGN )

两个锁存器构成一个触发器

- The storage elements (memory) used in clocked sequential circuits are called *flipflops*.
- The most economical and efficient flip-flop constructed is the edge-triggered *D flipflop*, because it requires the smallest number of gates.


 


Figure for master-slave **positive-edge** triggered **D flip-flop**


```
module D_ff_p_from_latch(  
    input clk, D,  
    output Q  
);  
    /*module D_latch( input En,D,  
        output reg Q, output nQ );*/  
    wire P, nq_master, nq_slaver;  
    D_latch ud_master(~clk, D, P,nq_master);  
    D_latch ud_slaver(clk, P, Q, nq_slaver);  
endmodule
```
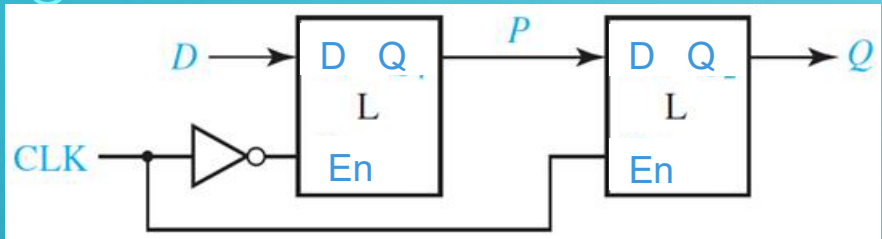
# FLIP FLOP ( TESTBENCH, WAVEFORM )

master-slave **positive-edge** triggered D flip-flop


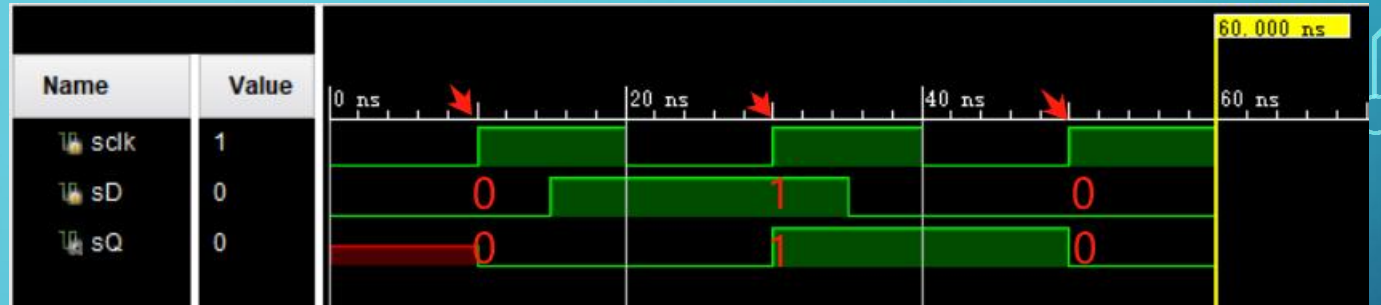
```
module D_ff_p_from_latch(
input clk, D,
output Q
);
/*module D_latch( input En,D,
output reg Q, output nQ );*/
wire P, nq_master, nq_slaver;
D_latch ud_master(~clk, D, P,nq_master);
D_latch ud_slaver(clk, P, Q, nq_slaver);
endmodule
```




```
module D_ff_p_tb( );
/*module D_ff_p_from_latch(input clk, D, output Q );*/
reg sclk, sD;
wire sQ;
D_ff_p_from_latch dut1(sclk, sD, sQ);
initial begin
sclk=1'b0;
forever #10 sclk = ~sclk;
end
initial fork
sD = 1'b0;
#15 sD = 1'b1;
#35 sD = 1'b0;
#60 $finish;
join
endmodule
```



# D FLIP FLOP

| Clk | Q         |
|-----|-----------|
| ↑   | D         |
| 0   | no change |
| 1   | no change |
| ↓   | no change |

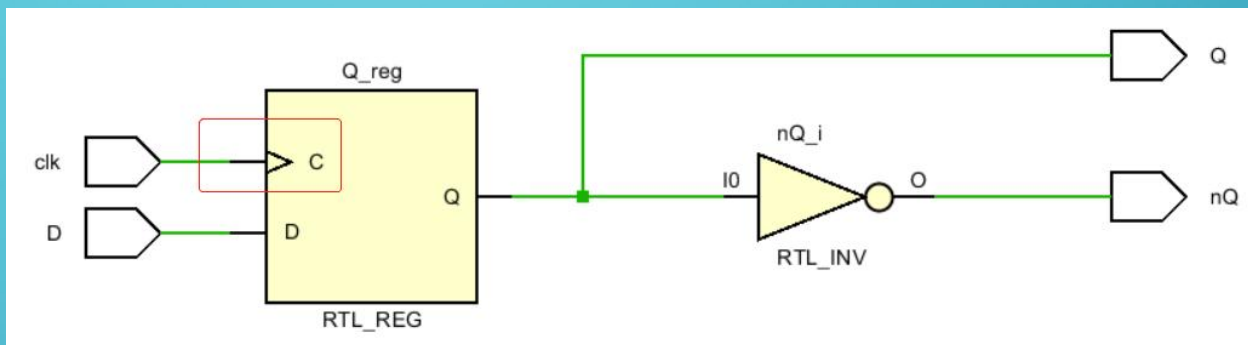Here is **positive-edge** triggered D flip-flop




组合逻辑里用阻塞赋值=  
时序电路里用非阻塞赋值<=  
例：  
begin  
a=b;  
b=a;  
end  
结果：  
a==b  
begin  
a<=b;  
b<=a;  
end  
a、b交换b==b

```
module D_flipflop(
    input clk, D,
    output reg Q,
    output nQ
);
    always @(posedge clk)
        Q <= D;
    assign nQ = ~Q;
endmodule
```


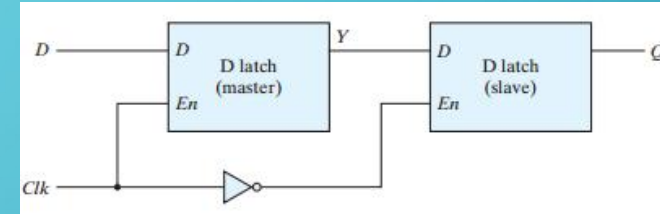
# PRACTICE(1)

- Implement a negative-edge triggered D flipflop
  - a) by using two D latch
  - b) using behavior manner



- Build a testbench to test the negative-edge triggered D flipflop, do the simulation.
  - the expected waveform of the negative-edge triggered D flipflop is shown in the following figure.




# JK FLIP FLOP(1)

- $$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

次态
现态

| J | K | $Q^{n+1}$ |
|---|---|-----------|
| 0 | 0 | no change |
| 0 | 1 | 0 reset   |
| 1 | 0 | 1 set     |
| 1 | 1 | $Q^n$     |

| JK    |   | 00 | 01 | 11 | 10 |
|-------|---|----|----|----|----|
| $Q^n$ | 0 | 0  | 0  | 1  | 1  |
|       | 1 | 1  | 0  | 0  | 1  |

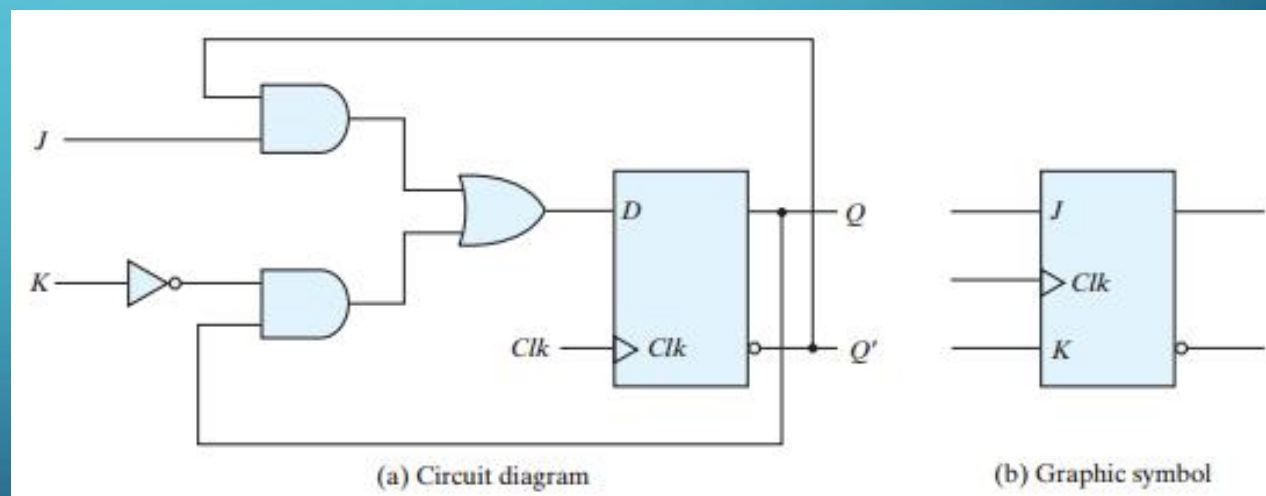

# JK FLIP FLOP(2)

$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

```
module J_K_Flip_Flop(
    input Clk, J, K,
    output reg Q,
    output nQ
);
    assign nQ = ~Q;
    always @ (posedge Clk)
        case ({J, K})
            2'b10: Q<= 1'b1; //set
            2'b01: Q<= 1'b0; //reset
            2'b11: Q<= nQ; //reverse
            2'b00: Q<= Q; //keep
        endcase
endmodule
```

| J | K | Q <sup>n+1</sup> |
|---|---|------------------|
| 0 | 0 | no change        |
| 0 | 1 | 0                |
| 1 | 0 | 1                |
| 1 | 1 | Q <sup>n'</sup>  |



# USING JK FLIP FLOP TO IMPLEMENT D FLIP FLOP


- JK Flip-Flop:  $Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$
- D Flip-Flop:  $Q^{n+1} = D = D\overline{Q}^n + DQ^n$

| J | K | $Q^{n+1}$ |
|---|---|-----------|
| 0 | 0 | no change |
| 0 | 1 | 0         |
| 1 | 0 | 1         |
| 1 | 1 | $Q^n$     |

| Clk | Q         |
|-----|-----------|
| ↑   | D         |
| 0   | no change |
| 1   | no change |
| ↓   | no change |

```

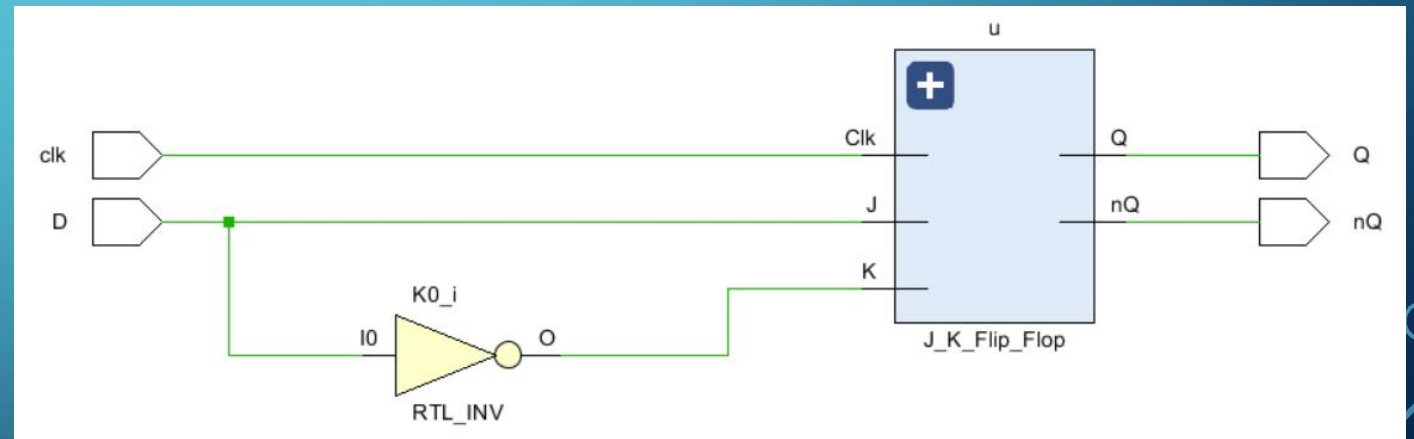
module Dff_byJKff(
input clk, D,
output Q, nQ
);
    J_K_Flip_Flop u(clk, D, ~D, Q, nQ);
endmodule
    
```




 
# T FLIP FLOP

- The  $T$  (toggle) flip-flop is a complementing flip-flop.




| $T$ | $Q^{n+1}$  |
|-----|------------|
| 0   | $Q^n$      |
| 1   | $\sim Q^n$ |

```
module T_Flip_Flop(  
    input Clk, T,  
    output reg Q,  
    output nQ  
);  
    assign nQ = ~Q;  
    always @(posedge Clk)  
        case(T)  
            1'b1: Q<= ~Q;  
            1'b0: Q<= Q;  
        endcase  
endmodule
```
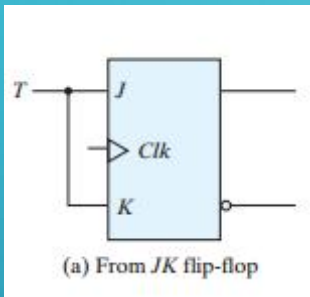
# USING JK FLIP FLOP TO IMPLEMENT T FLIP FLOP


- The  $T$  (toggle) can be obtained from a  $JK$  flip-flop when inputs  $J$  and  $K$  are tied together.



| $T$ | $Q^{n+1}$  |
|-----|------------|
| 0   | $Q^n$      |
| 1   | $\sim Q^n$ |

| $J$ | $K$ | $Q^{n+1}$ |
|-----|-----|-----------|
| 0   | 0   | no change |
| 0   | 1   | 0         |
| 1   | 0   | 1         |
| 1   | 1   | $Q^n$     |
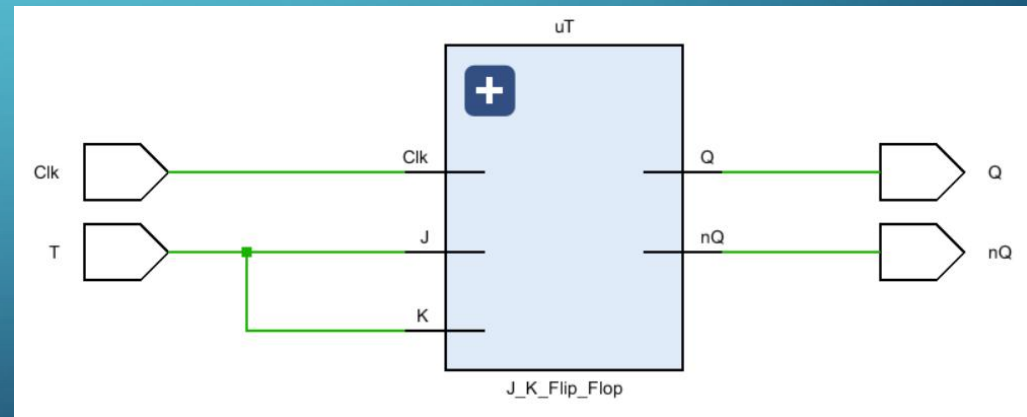
```
module Tff_by_JKff(  
    input Clk, T,  
    output Q, nQ  
);  
    J_K_Flip_Flop uT( Clk, T, T, Q, nQ);  
endmodule
```



# WIRE VS REG(1)

- There are two data types in Verilog: **wire** and **register**.
  - **wire** is a kind of net, which is equivalent to physical connection.
  - **wire** is used to connects two points, and thus does **not have any driving strength**
  - **wire** data types can be used for connecting the output port to the actual driver
  - a **wire** can be assigned a value by a continuous assign statement, which is used for **designing combinational logic**
  - **default data type is wire**: this means that if you declare a port or variable without specifying reg or wire, it will be a 1-bit wide wire.
  - **reg** is a kind of register, which is equivalent to memory cell.
  - reg can **store value and drive strength**. Reg can be used for **modeling both combinational and sequential logic**.
  - **reg** data type can be driven from initial and always block.
  - The LHS of a **behavioral block(initial , always)** should be declared **as reg**
  - **input port** could drive by both wire/register, but it could ONLY be declared as wire
  - **output port** can be declared as wire or register, but it can ONLY drive wire
  - **bidirectional port** can only be declared as wire

# NON-BLOCKING ASSIGNMENT VS BLOCKING ASSIGNMENT

- The '=' token represents a **blocking procedural assignment**
- A **combinational logic always block** should use **Blocking assignments**("=").
- The '<=' token represents a **non-blocking procedural assignment**
- A **sequential logic always block** should use **Non-blocking assignments**("<=").

**NOTE: DO NOT** mixing blocking assignment and non-blocking assignment in the same always block !!!

## PRACTICE(2)

- Try to construct a T flipflop with a reset input.
  - There would be a reset input port apart from other inputs(clk, T), while it enable the output of T flipflop is 1'b0, while it disable the circuit works as T flipflop
  - Do the design and verify the function of your design.
  - Create the constraint file, do the synthetic and implementation, generate the bitstream file and program the device, then test on the minisys develop board.



## PRACTICES(3)

$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$


- Can this JK flip-flop work?
- Try to use it implement a T flip-flop, do the design, create constraint file, generate the bitstream file and program the device.
- Can the T flip-flop work? Explain the reason.

缺少else分支

```
module J_K_Flip_Flop(  
    input Clk, J, K,  
    output reg Q, Qn  
);  
    always @(posedge Clk)  
        if({J, K} == 2'b10) //set  
            begin  
                {Q, Qn} <= 2'b10;  
            end  
        else if ({J, K} == 2'b01) //reset  
            begin  
                {Q, Qn} = 2'b01;  
            end  
        else if ({J, K} == 2'b11) //reverse  
            begin  
                Q <= Qn;  
                Qn <= Q;  
            end  
        end  
endmodule
```
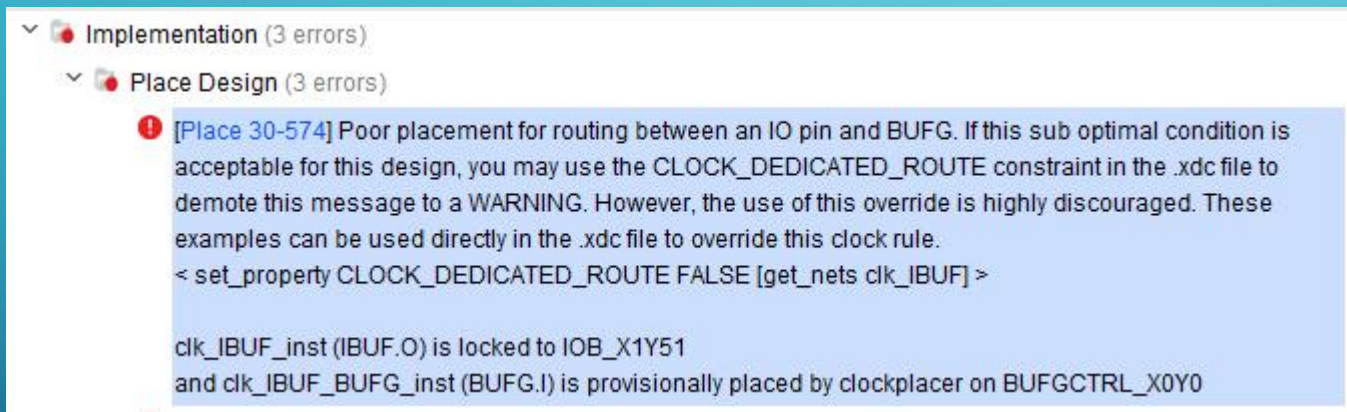
# TIPS:

- Constraints: if you want to use IO pin as clock, you should use the `CLOCK_DEDICATED_ROUTE FALSE` constraint in the .xdc file to demote the Error message to a (Critical) WARNING. NOTES: This (Critical) WARNING HERE could be ignored.



```
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports D]
set_property IOSTANDARD LVCMOS33 [get_ports Q]
set_property IOSTANDARD LVCMOS33 [get_ports Qn]
set_property PACKAGE_PIN P5 [get_ports clk]
set_property PACKAGE_PIN R1 [get_ports D]
set_property PACKAGE_PIN J2 [get_ports Q]
set_property PACKAGE_PIN K2 [get_ports Qn]
set_property CLOCK DEDICATED ROUTE FALSE [get_nets {clk IBUF}]
```